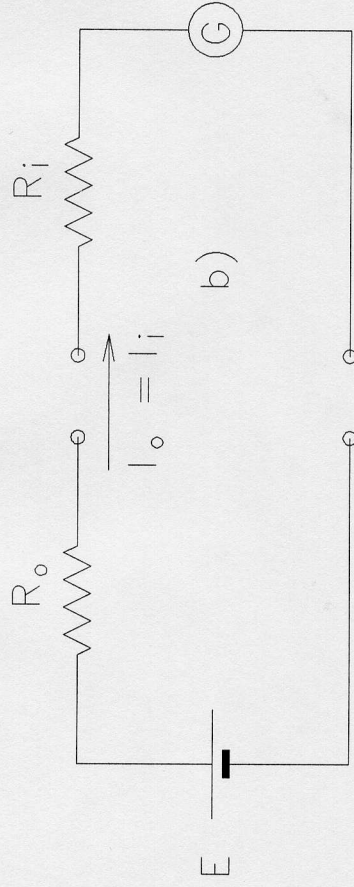


Since E is a "perfect" voltage source it remains constant under any load.

Therefore $E = E_o$, the open circuit voltage.



In order that the actual circuit a) be equivalent to the Thévenin equivalent b) the current I_i through the instrument G must be the same in both cases.

$$a) I_p = E/R_p = E_o/R_p, I_i = E/R_i = E_o/R_i$$

$$b) I_o = I_i = E/(R_o + R_i) = E_o/(R_o + R_i)$$

Since I_i must be the same in both a) and b) we see $R_i = R_o + R_o$ or $R_o = 0$.

$$(26) \text{TEq41g}$$