

lecture 3

Combinational logic 1

- truth tables
- Boolean algebra
- sum of products and product-of-sums
- logic gates

January 18, 2016

Quiz 1

Class should start after ~15 min.

Let A, B be binary variables

("boolean")

$1 \equiv \text{true}$, $0 \equiv \text{false}$

Notation: $A \cdot B \equiv A \text{ and } B$

$A + B \equiv A \text{ or } B$

$\bar{A} \equiv \text{not } A$

One uses $+, \cdot$ instead of \vee, \wedge .
which you may have seen elsewhere.


Truth Tables

Notation: $A \cdot B \equiv A \text{ and } B$

$A + B \equiv A \text{ or } B$

$\bar{A} \equiv \text{not } A$

A	B	$A \cdot B$	$A + B$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

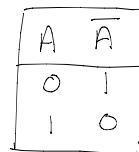

NAND NOR (exclusive or)

A	B	$\overline{A \cdot B}$	$\overline{A+B}$	$A \oplus B$
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	0	0	0

There are $2^4 = 16$ possible boolean functions.

$$f: \{0,1\} \times \{0,1\} \rightarrow \{0,1\}$$

A	B	y_1	y_2	y_3	...	y_{16}
0	0					
0	1					
1	0					
1	1					

We typically only work with AND, OR, NAND, NOR, XOR.

Laws of Boolean Algebra

identity

$$A + 0 = A \quad A \cdot 1 = A$$

inverse

$$A + \bar{A} = 1 \quad A \cdot \bar{A} = 0$$

one and zero

$$A + 1 = 1 \quad A \cdot 0 = 0$$

commutative

$$A + B = B + A \quad A \cdot B = B \cdot A$$

associative

$$(A + B) + C = A + (B + C) \quad (A \cdot B) \cdot C = A \cdot (B \cdot C)$$

distributive

$$A \cdot (B + C) = (A \cdot B) + (A \cdot C) \quad A + (B \cdot C) = (A + B) \cdot (A + C)$$

de Morgan

$$(\overline{A + B}) = \bar{A} \cdot \bar{B} \quad \overline{A \cdot B} = \bar{A} + \bar{B}$$

Laws of Boolean Algebra

distributive

$$A + (B \cdot C) = (A + B) \cdot (A + C)$$

Note this one behaves differently from integers or reals.

Example

$$Y = \overline{A \cdot B \cdot C} \cdot (A \cdot \bar{B} + A \cdot C)$$

A	B	C	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

$$Y = \overline{A \cdot B \cdot C} \cdot (A \cdot B + A \cdot C)$$

A	B	C	$A \cdot B \cdot C$	$\overline{A \cdot B \cdot C}$	$A \cdot B$	$A \cdot C$	$A \cdot B + A \cdot C$	Y
0	0	0	0	1	0	0	0	0
0	0	1	0	1	0	0	0	0
0	1	0	0	1	0	0	0	0
0	1	1	0	1	0	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	0	1	0	1	1	1
1	1	0	0	1	1	0	1	1
1	1	1	1	0	1	1	1	0

How to write Y as a "product of sums" ?

First, write its complement \overline{Y} as a sum of products.

Because of time constraints, I decided to skip this example in the lecture.

You should go over it on your own.

A	B	C	Y	\overline{Y}
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	0	1

$$\overline{Y} = \overline{A \cdot B \cdot C} + \overline{A \cdot \overline{B} \cdot C} + \overline{A \cdot B \cdot \overline{C}} + \overline{A \cdot \overline{B} \cdot \overline{C}} + A \cdot \overline{B} \cdot C$$

Sum of Products

$$Y = \overline{A \cdot B \cdot C} \cdot (A \cdot B + A \cdot C)$$

$$= A \cdot \overline{B} \cdot C + A \cdot B \cdot \overline{C}$$

Q: For 3 variables A, B, C, how many terms can we have in a sum of products representation ?

A: $2^3 = 8$ i.e. previous slide

$$Y = A \cdot \overline{B} \cdot C + A \cdot B \cdot \overline{C}$$

$$\overline{Y} = \overline{A \cdot \overline{B} \cdot C} + \overline{A \cdot B \cdot \overline{C}}$$

$$= (\overline{A \cdot \overline{B} \cdot C}) \cdot (\overline{A \cdot B \cdot \overline{C}})$$

$$= (\overline{A} + \overline{B} + \overline{C}) \cdot (\overline{A} + \overline{B} + C)$$

called a "product of sums"

Sometimes we have expressions where various combinations of input variables give the same output. In the example below, if A is false then any combination of B and C will give the same output (namely true).

$$Y = A \cdot \overline{B} \cdot C + \overline{A}$$

A	B	C	$A \cdot \overline{B} \cdot C$	\overline{A}	Y
0	0	0	0	1	1
0	0	1	0	1	1
0	1	0	0	1	1
0	1	1	0	1	1
1	0	0	0	0	0
1	0	1	1	0	1
1	1	0	1	0	0
1	1	1	0	0	0

Don't Care

We can simplify the truth table in such situations.


$$Y = A \cdot \overline{B} \cdot C + \overline{A}$$

A	B	C	Y
0	X	X	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

X means we "don't care" what values are there.


What are the 0's and 1's in a computer?

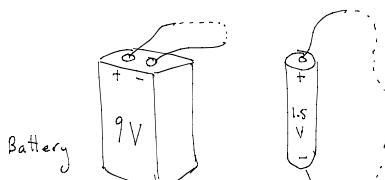A wire can have a voltage difference between two terminals, which drives current.



In a computer, wires can have two voltages:
high (1, current ON) or low (0, current ~OFF)

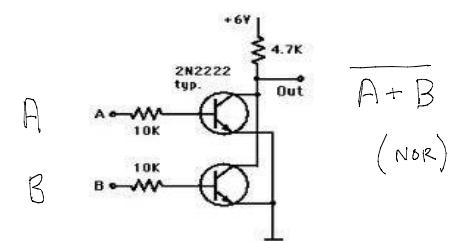Using circuit elements called "transistors" and "resistors", one can build circuits called "gates" that compute logical operations.



For each of the OR, AND, NAND, XOR gates, you would have a different circuit.

Moore's Law (Gordon Moore was founder of Intel)



The number of transistors per mm² approximately doubles every two years. (1965)

It is an observation, not a physical law.

It still holds true today, although people think that this cannot continue, because of limits on the size of atom and laws of quantum physics.

<http://phys.org/news/2015-07-law-years.html>


Logic Gates

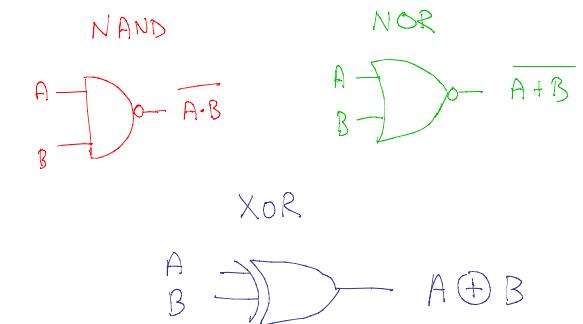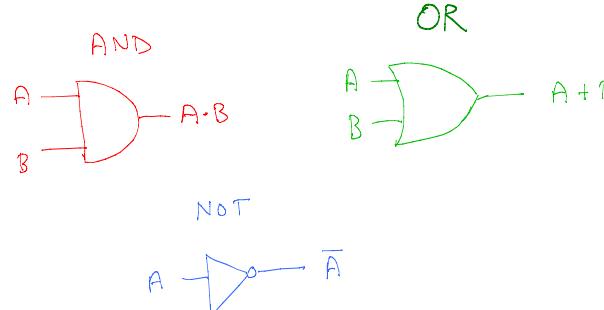

Logic Circuit


Example:

$$Y = \overline{A \cdot B} + A \cdot C$$

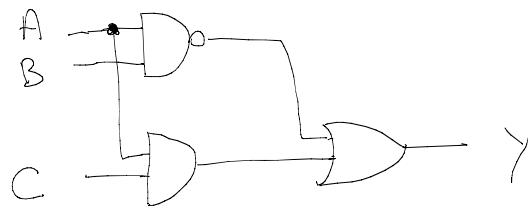

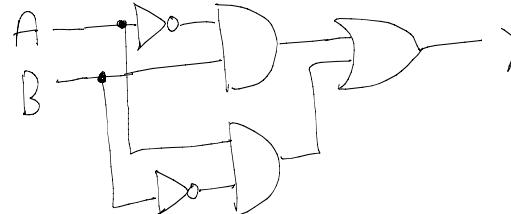
Example: XOR without using an XOR gate

$$Y = \overline{A \cdot B} + A \cdot \overline{B} = A \oplus B$$



Multiplexor (selector)


$$Y = \overline{S} \cdot A + S \cdot B$$

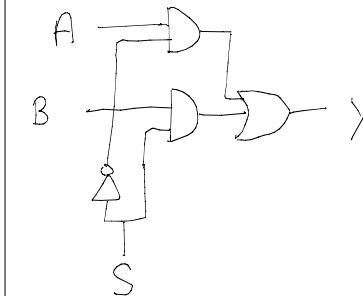

if S
Y = B
else
Y = A


Notation

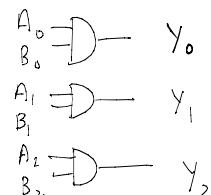Suppose A and B are each 3 bits ($A_2 A_1 A_0$, $B_2 B_1 B_0$)



Suppose A and B are each 8 bits ($A_7 A_6 \dots A_0$, $B_7 B_6 \dots B_0$)
We can define an 8 bit multiplexor (selector).

Notation:

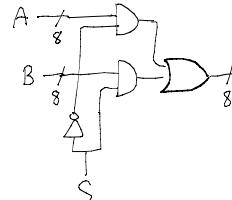

In fact we would build this from 8 separate one-bit multiplexors.

Note that the selector S is a single bit. We are selecting either all the A bits or all the B bits.

Announcement

The enrollment cap will be lifted before DROP/ADD to allow students on the waitlist to register.