

lecture 4

Combinational logic

Last lecture

- truth tables
 - $Y = f(A, B, \dots)$
 - sums of products
- logical gates & circuits



Arithmetic Circuits

$$\begin{array}{r}
 C_{n-1} \dots C_2 C_1 C_0 \\
 A_{n-1} \dots A_2 A_1 A_0 \\
 + B_{n-1} \dots B_2 B_1 B_0 \\
 \hline
 S_{n-1} \dots S_2 S_1 S_0
 \end{array}$$

Note

- $C_0 = 0$
- A, B could be positive or negative

Sum of products? \Rightarrow fast 😊

| $B_{31} A_{31} \dots B_1 A_1 B_0 A_0$ | $S_{31} \dots S_2 S_1 S_0$ |
|---------------------------------------|----------------------------|
| 2^{32-2} | |
| rows | |

$\sim 2^{2 \times 32}$ gates \Rightarrow big 😞

$$\begin{array}{r}
 C_{n-1} \dots C_2 C_1 \\
 A_{n-1} \dots A_2 A_1 A_0 \\
 B_{n-1} \dots B_2 B_1 B_0 \\
 \hline
 S_{n-1} \dots S_2 S_1 S_0
 \end{array}$$

| $A_0 B_0$ | $S_0 C_1$ |
|-----------|-----------|
| 0 0 | 0 0 |
| 0 1 | 1 0 |
| 1 0 | 1 0 |
| 1 1 | 0 1 |


$$S_0 = A_0 \oplus B_0$$

$$C_1 = A_0 \cdot B_0$$

Half Adder

$$S = A \oplus B$$


$$C = A \cdot B$$

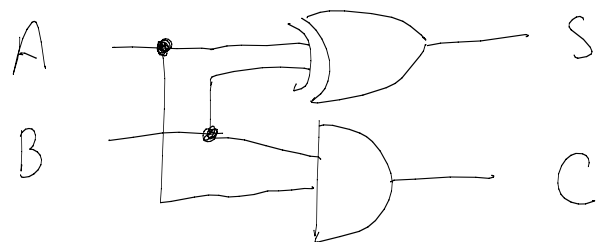


$C_{n-1} \dots C_2 C_1 C_0$
 $A_{n-1} \dots A_2 A_1 A_0$
 $B_{n-1} \dots B_2 B_1 B_0$

 $S_{n-1} \dots S_2 S_1 S_0$

| A_k | B_k | C_k | S_k | C_{k+1} |
|-------|-------|-------|-------|-----------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

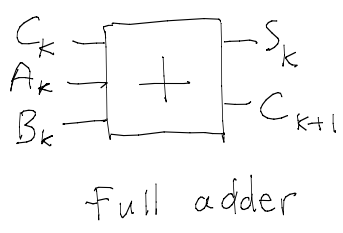


Ripple Adder

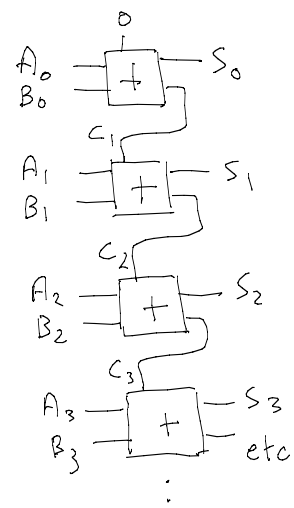

If $n=32$, we can have a long delay as carries propagate through the circuit.

☹️
we'll return to this later.

Overflow

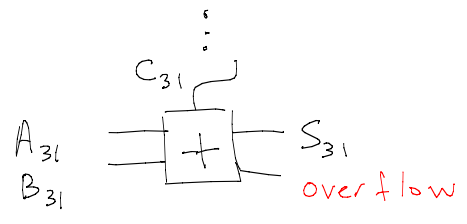

| | | | |
|----------|----------|----------|----------|
| A_{31} | B_{31} | S_{31} | overflow |
|----------|----------|----------|----------|


See Exercises 2

Encoder

| | |
|-------------------------|-----------------|
| $A_m \dots A_2 A_1 A_0$ | $Y_n \dots Y_0$ |
| | |

events (many bits) code word (few bits)

Encoder: Example 1

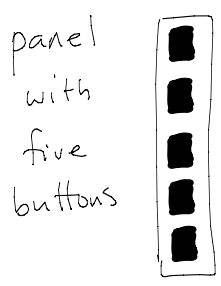


| b_4 | b_3 | b_2 | b_1 | b_0 | Y_2 | Y_1 | Y_0 |
|-------|-------|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |

Suppose only one pressed at any time

Q: What if two buttons are pressed at same time?

A: none of lights go on.
(assuming a sum-of-products implementation of each L_i)

panel with five buttons

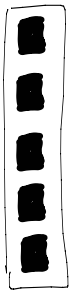


| b_4 | b_3 | b_2 | b_1 | b_0 | Y_2 | Y_1 | Y_0 |
|-------|-------|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| x | x | x | x | 1 | 0 | 0 | 1 |
| x | x | x | 1 | 0 | 0 | 1 | 0 |
| x | x | 1 | 0 | 0 | 0 | 1 | 1 |
| x | 1 | 0 | 0 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 1 | 0 | 1 |


Allow any number of buttons to be pressed.

Encoder: Example 2

panel with ten buttons

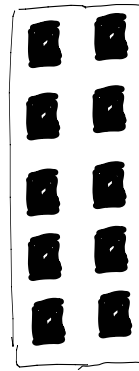

$b_9 \dots b_0$

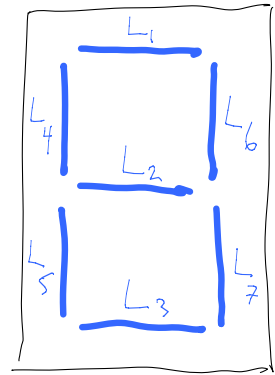



| b_9 | b_0 | $L_7 L_6 \dots L_2 L_1$ |
|-------|-------|-------------------------|
| 0 | 1 | see Exercises 2 |
| 1 | 0 | |

Decoder


| $b_2 b_1 b_0$ | Y_7 | \dots | Y_2 | Y_1 | Y_0 |
|---------------|-------|---------|-------|-------|-------|
| 0 0 0 | 1 | | | | |
| 0 0 1 | | | | | 0 |
| 0 1 0 | | | | | |
| 0 1 1 | | | | | |
| 1 0 0 | | | | | |
| 1 0 1 | | | | | |
| 1 1 0 | | | | | |
| 1 1 1 | | | | | |

Code word

events

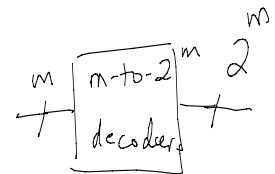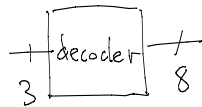


Multiplexor (also called selector)

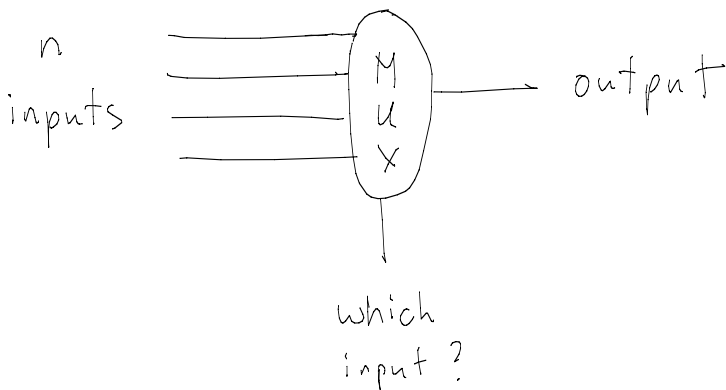



1-bit multiplexor

$$Y = \bar{S} \cdot A + S \cdot B$$

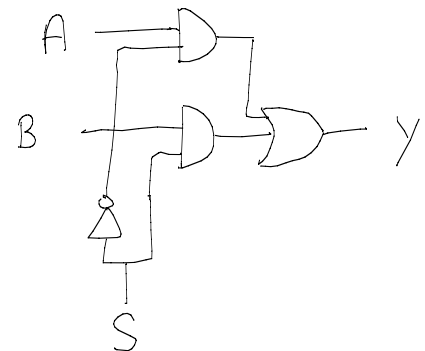


2-bit multiplexor

(What is the circuit?)

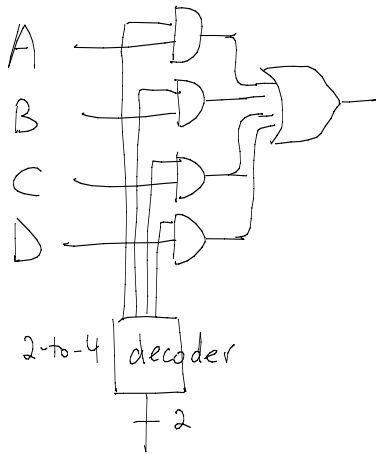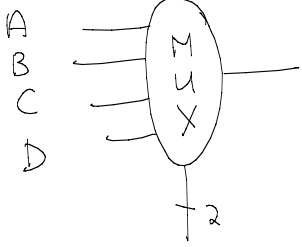

2-bit multiplexor

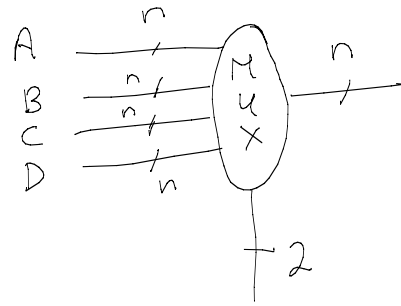


Selects from four n -bit inputs. For each $A_i B_i C_i D_i$, replicate circuit on previous slide (but use same decoder).


Ripple Adder

Recall arithmetic circuit

slow!


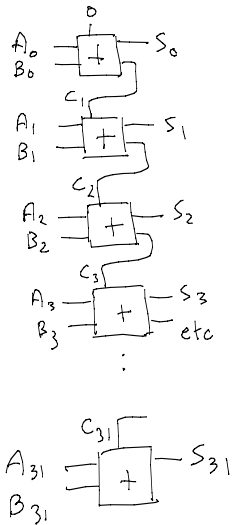


How to speed up the adder?

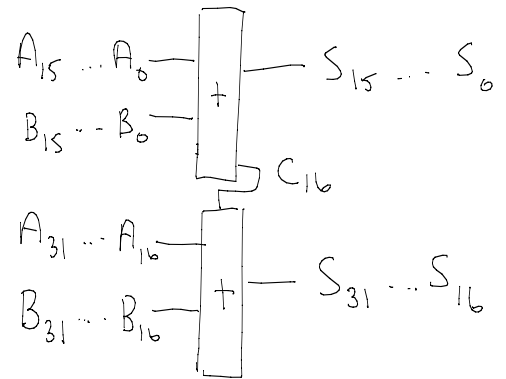


Does this speed it up? No.

"Conditional Sum" Adder

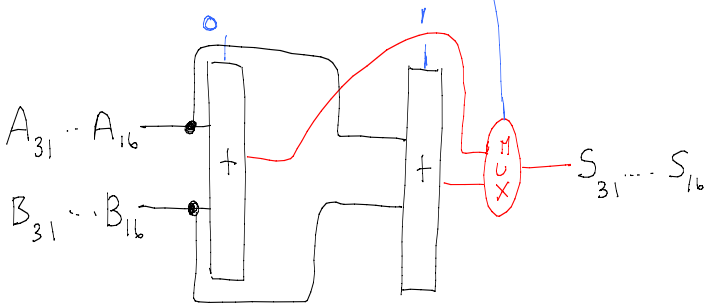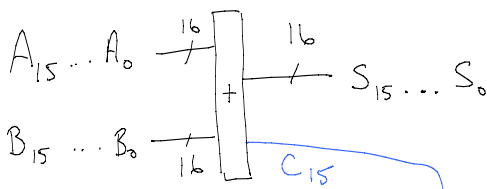

Many adders have been proposed:

small, slow

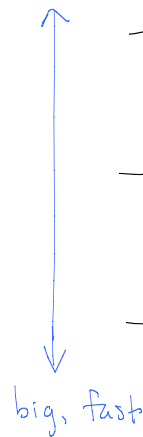




- ripple
- ⋮
- conditional sum (previous slide shows basic idea only)
- ⋮
- sum of products

Subtraction

$$\begin{array}{r}
 A_{n-1} \dots A_2 A_1 A_0 \\
 - B_{n-1} \dots B_2 B_1 B_0 \\
 \hline
 S_{n-1} \dots S_2 S_1 S_0
 \end{array}$$


$$x - y = x + (-y)$$

↑
invert bits and add 1

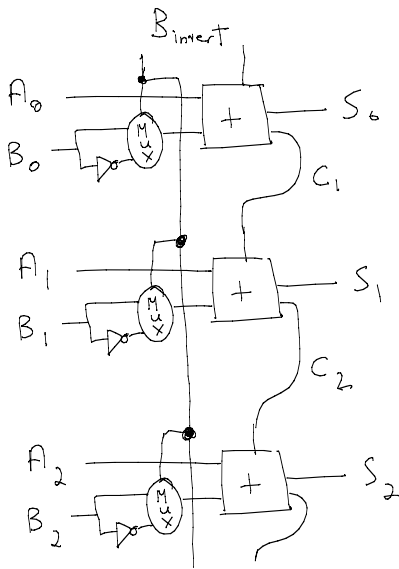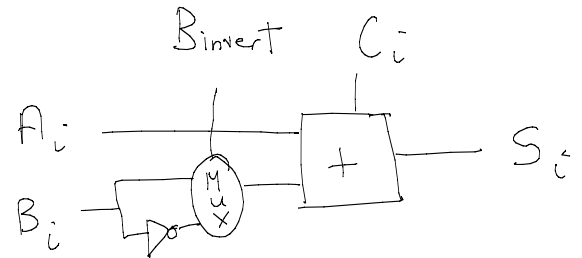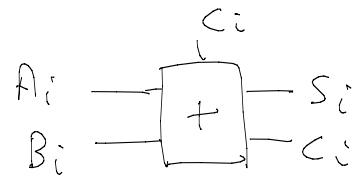


$$\begin{array}{r}
 A_{n-1} \dots A_2 A_1 A_0 \\
 B_{n-1} \dots B_2 B_1 B_0 \\
 \hline
 S_{n-1} \dots S_2 S_1 S_0
 \end{array}$$

$n = 32$

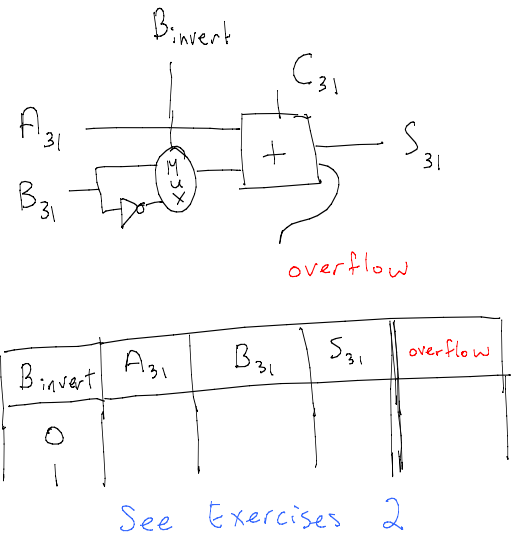

More operators:
bit-wise AND, OR

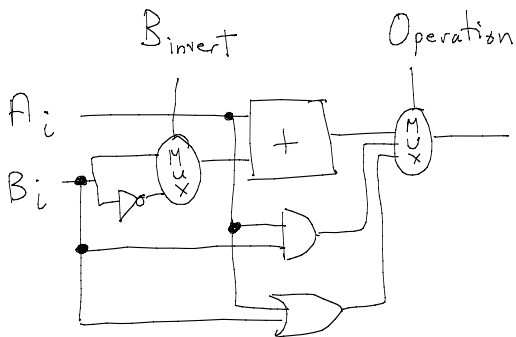

the fast adder implementation
to the adder part

Arithmetic Logic Unit (ALU)

