 



General Purpose 1-bit

1. Incrementer
2. Decrementer
3. 1/2-Adder
4. 1/2-Subtractor





3x3=6 bit PARALLEL MULTIPLIER


Regular Architecture

 

Minimal Architecture

 

 


 


16-bit to 8-bit parallel square-rooter

Elements of Sequential Circuits


NAND Flip-Flop

 


Gated Flip-Flop

 


J-K Flip-Flop (Race problem)

 


NOR Flip-Flop

 


SOC (Set overrides Clear)

 


Master/Slave Data Flip-Flop

 


Low going falling edge trigger

 

Can it be done with NOR-gates?

 

Low going rising edge trigger

 

+

